

<https://www.youtube.com/watch?app=desktop&v=SwQkadpjZJE>

YouTube
Artigiano 2.0 - Alessio Romanelli · 5:55

The diagram illustrates the electrical connections for a stepper motor system. A 24V 15A power supply is connected to the TB 6560 V2.0 driver board. The driver board is connected to a stepper motor. An Arduino Uno is connected to the driver board via its digital pins. A +9V battery is also connected to the system. The connections are as follows:

- Power Supply (24V 15A) to TB 6560 V2.0 driver board.
- Stepper Motor to TB 6560 V2.0 driver board.
- Arduino Uno to TB 6560 V2.0 driver board (Digital pins).
- +9V battery to the system.
- Pin 8 (STEP) to Arduino.
- Pin 9 (DIR) to Arduino.
- GND connection.

STEPPER MOTOR AND ARDUINO EASY DRIVING WITH TB 6560 V2.0 DRIVER

Ansehen >

Hochgeladen: 26.02.2019 · 15.707 Aufrufe · 121 Positive Bewertungen

How to move a stepper motor in a very simple way, with Arduino and a single-axis tb-6560 driver board., file... [Mehr](#) ▾

Bilder sind in der Regel urheberrechtlich geschützt. Weitere Infos

From:
<https://wiki.fbetechn.de/> - hls-Planung

Permanent link:
https://wiki.fbetechn.de/doku.php?id=privat:projekte:cnc:bl-tb6560_steppermotor:steppermotor&rev=1768843266

Last update: 2026/01/19 17:21

